

26.41. In the circuit shown in Fig. 26.58 both capacitors are initially charged to 45.0 V. (a) How long after closing the switch S will the potential across each capacitor be reduced to 10.0 V, and (b) what will be the current at that time?

Figure 26.58

Exercise 26.41.

