

**31.41.** A coil has a resistance of  $48.0\ \Omega$ . At a frequency of  $80.0\ \text{Hz}$  the voltage across the coil leads the current in it by  $52.3^\circ$ . Determine the inductance of the coil.