

3-3)

- A) Calculate the effective capacitance of the combination shown.
- B) If a potential difference of 16 Volts is applied across the ends of the combination, how much charge is 'on' each capacitor?

