

4-4)

Find the current through each of the resistors. Be sure to indicate the directions (perhaps left/right/top of page/bottom of page).

