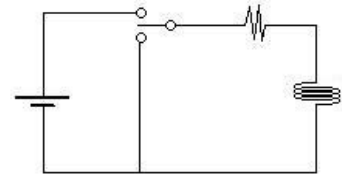


6-5)

Consider an LR circuit with a battery, \mathcal{E}_B . The circuit has been running for a very long time. The battery is removed at $t = 0$ and the rest of the circuit immediately reconnected. Five milliseconds later, the current is measured to be 0.2 A. If $R = 15 \text{ Ohms}$ and the *emf* of the battery is 12 V,



- A) What is the inductance, L ?
- B) What is the time constant, τ_L ?
- C) How long after the switch is thrown will the voltage across the resistor be 4V?