

6-8)

In a series LRC circuit, the phase angle is 62° , the resistance is 24 Ohms, the capacitance reactance is 38 Ohms, and the AC *emf* is 5 Volts.

- A) Find the inductive reactance.
- B) What is the maximum current in the circuit?