

6-9)

A capacitor, an inductor, and a resistor are connected in series with a sinusoidal AC *emf*. At what frequency  $\omega$  will the maximum voltage drop across the inductor,  $(V_{L\text{ MAX}})_{\text{MAX}}$ , itself be maximized? This is a tedious one.