

6-8 Soln)

A)

$$\tan \varphi = \frac{\chi_L - \chi_C}{R}$$

$$\chi_L = R \tan \varphi + \chi_C = 24(\tan(62^\circ)) + 38 = 83.1 \, \Omega$$

B)

$$I_{\text{MAX}} = \frac{\mathcal{E}_{\text{MAX}}}{Z} = \frac{\mathcal{E}_{\text{MAX}}}{\sqrt{R^2 + (\chi_L - \chi_C)^2}} = \frac{5}{\sqrt{24^2 + (83 - 38)^2}} = 0.098 \text{ Amps}$$